

**G-3/388/22**

Roll No. ....

**III Semester Examination, January, 2022**

**M.Sc.**

**PHYSICS**

**Paper IV**

**(Photonics and Op Amp)**

Time : 3 Hours ]

[ Max. Marks : 80

**Note :** *All questions are compulsory. Question Paper comprises of 3 Sections. Section A is objective type/multiple choice questions with no internal choice. Section B is short answer type with internal choice. Section C is long answer type with internal choice.*

**SECTION A**

**1×8=8**

**(Objective Type/Multiple Choice Questions)**

Choose the correct answer :

- 1.** An LED, radiation is in :  
(a) Visible region  
(b) Infrared region  
(c) Visible and infrared region  
(d) Neither visible nor infrared region
- 2.** An infrared LED is usually fabricated from :  
(a) Ge                      (b) Si  
(c) GaAs                  (d) GaAsP

P.T.O.

[ 2 ]

- 3.** Which one of the following photodetector does not provide gain ?  
(a) Phototransistor  
(b) Photoconductor  
(c) Avalanche photodiode  
(d) *p-i-n* photodiode
- 4.** A solar cell operated on the principle of :  
(a) Recombination      (b) Photovoltaic effect  
(c) Diffusion              (d) Thermoelectric effect
- 5.** An differential gain is :  
(a) Very high  
(b) Very low  
(c) Dependent on input voltage  
(d) Zero
- 6.** A differential amplifier is :  
(a) is a part of an OP-AMP  
(b) has one input and one output  
(c) has two outputs  
(d) Both (a) and (c)
- 7.** The phase in the integrator and differentiator circuit respectively are :  
(a)  $+ 90^\circ$  and  $+ 90^\circ$     (b)  $+ 90^\circ$  and  $- 90^\circ$   
(c)  $- 90^\circ$  and  $+ 90^\circ$     (d)  $- 90^\circ$  and  $- 90^\circ$

**G-3/388/22**

[ 3 ]

8. If a square wave is applied to the input of an OP AMP integrator circuit, the output would be :

- (a) sine wave                      (b) triangular wave  
(c) pulse                              (d) ramp

**SECTION B**

**6×4=24**

**(Short Answer Type Questions)**

**Unit-I**

1. Explain radiative and non-radiative transitions.

*Or*

Write the advantages and disadvantages of LEDs.

**Unit-II**

2. Derive the expression for gain of the photoconductive detector.

*Or*

Write the advantages and limitations of Solar cells.

**Unit-III**

3. Draw schematic block diagram of the basic OP-AMP with inverting and non-inverting inputs. Sketch their equivalent circuits.

**G-3/388/22**

P.T.O.

[ 4 ]

*Or*

What is meant by an ideal difference amplifier ?

What are differential gain and common mode gain of a differential amplifier ?

**Unit-IV**

4. Discuss the two applications of summing amplifiers.

*Or*

Explain the operation of an OP-amp differentiator.

**SECTION C**

**12×4=48**

**(Long Answer Type Questions)**

**Unit-I**

1. Explain the construction and working of a Light Emitting diode.

*Or*

Write note on Photoconductive devices (LDR).

**Unit-II**

2. What is a phototransistor ? Explain its principle of operation and give its V-I Characteristics. What are the advantages and disadvantages of a phototransistor ?

**G-3/388/22**

*Or*

Write notes on the following :

- (a) Solar cells
- (b) P-N junction solar cells

**Unit-III**

- 3.** Explain DC analysis of dual input balanced differential amplifier.

*Or*

Describe voltage series feedback operational amplifier. Explain their different parameters.

*Or*

Sketch the circuit diagram of non-inverting amplifier with feedback and determine the expression for closed loop voltage gain, input resistance of OP-amp with feedback and output resistance with feedback.

**Unit-IV**

- 4.** Describe the principle of oscillator and its types. Draw the Wein Bridge Oscillator circuit and derive an expression for its frequency.

*Or*

What do you mean by multivibrator ? Discuss the circuit diagram and operation of a monostable multivibrator.

★ ★ ★ ★ ★ c ★ ★ ★ ★ ★