## Online Assignment, 2020

## B.Sc. Part -II

## **Information Technology**

## Paper -I

(Digital Circuits and Computer Hardware)

Time: 3 Hours]

[ Max. M.: 50

Note:- All Questions are Compulsory. All questions carry equal marks.

1. Explain Fix point and Floating point representation.

Or

Find the complement of the following function:

$$F = x' \cdot y + x \cdot (y' + z).$$

2. Explain BCD adder.

Or

Draw and explain T flip-flop.

3. Define Astable and Bistable multivibrator circuit.

Or

Write short note on RTL, DTL and TTL.

4. Describe instruction formats.

Or

Explain interrupt and their types.

**5.** Write the difference between primary memory and secondary memory.

Or

Explain Associative Memory.