

G-2/242/21

Roll No.

M.Sc. II Semester Examination, 2021

PHYSICS

Paper IV

(Digital Electronics)

Time : 3 Hours]

[Max. Marks : 80

Note : All questions are compulsory. Question Paper comprises of 3 sections. Section A is objective type/multiple choice questions with no internal choice. Section B is short answer type with internal choice. Section C is long answer type with internal choice.

SECTION A

1×10=10

(Objective Type Questions)

1. How many binary digits (bits) are required to represent decimal 15 ?
2. A product of sums expression leads to what kind of logic circuit ?
3. What is the meaning of 111_2 ? or 111_{10} ?
4. What is an encoder ?
5. What does an entry X-mean in a flip-flop truth table ?
6. What is the setup time for a 74164 shift register ?

P.T.O.

[2]

7. What is the LSB weight of a 6-bit resistive ladder ?
8. The most important advantage of an IC is its extremely high ?

SECTION B

6×4=24

(Short Answer Type Questions)

Note : Attempt one question from each unit.

Unit-I

1. Using 2's complement, solve the following :
(i) $110011 - 100111$ (ii) $101.1101 - 101.0111$

Or

Reduce the Boolean Function :

$$A\bar{B} + \bar{A}\bar{B} + AB + \bar{A}\bar{B}.$$

Unit-II

2. Describe the operation of Half and full adder.

Or

Discuss 4 : 1 multiplexer and 1 : 4 Demultiplexer.

Unit-III

3. Explain JK Flip-flop in detail.

Or

Write a notes on Shift Register.

G-2/242/21

Unit-IV

4. Explain R-2R ladder D/A converter.

Or

Write the fabrication of components on monolithic IC.

SECTION C**12×4=48****(Long Answer Type Questions)**

Note : Attempt one question from each unit.

Unit-I

1. Explain Universal Building Block gate and D'Morgan's law.

Or

Simplify the following logic function in SOP form using K-map and realise it by using minimum number of NAND gates and NOT gates.

$$F = \sum m (0, 2, 3, 5, 7, 8, 12, 13)$$

Unit-II

2. (a) Describe Ex-OR gates in detail.
(b) Draw 1's complement and 2's complements subtractor circuit.

Or

- (a) Explain DTL as a AND and OR gates.
(b) Discuss Transistor-Transistor Logic (TTL).

Unit-III

3. (a) Describe RS-flip-flop using UBB gates in detail.
(b) Discuss JKMSFF in detail.

Or

Explain Binary ripple counter and Ring counter in detail with time diagram.

Unit-IV

4. (a) Explain Successive approx. A/D converter.
(b) Write the applications of DACs and ADCs.

Or

- (a) Describe the Basic technology of monolithic IC.
(b) Define the scale of integration.

★ ★ ★ ★ ★ c ★ ★ ★ ★ ★